

BE87 FRESHMAN SEMINAR


WEEK 3: ECG AMPLIFIER DESIGN

- Electronic circuit for amplifying a biopotential
 - Functions of the circuit, parts summary
 - Discrete components in the design
-

GOALS FOR THIS LAB

- Review schematic design and function
 - Label your tool box and component boxes
 - Locate and organize electronic components:
 - Find resistors, capacitors, IC's, etc., place in plastic bag
 - Verify other components: breadboard with BNC-type connectors, ECG input wires, breadboard prototyping wires, batteries, battery holders
 - Create a parts list (with images or drawings) of your parts
-


ECG AMPLIFIER SCHEMATIC DESIGN

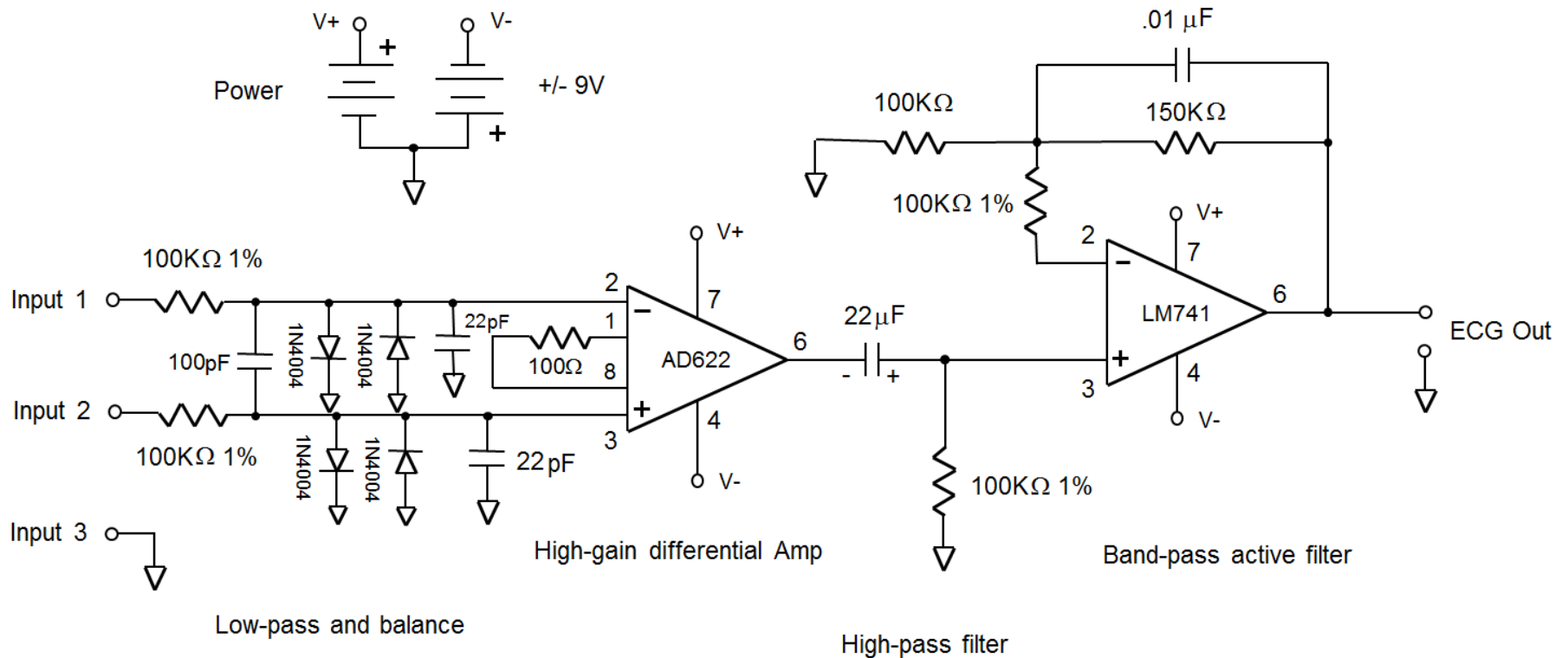

Note: the triangles  connected to components denote a connection to "ground" or a common wire.

FUNCTIONS OF THE CIRCUIT

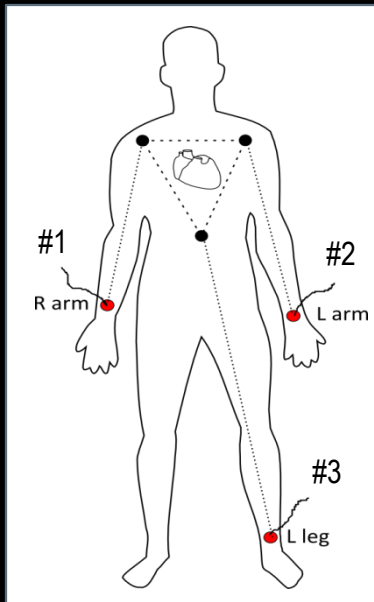- Input: ECG signal from a human subject
 - 3 wire/electrode inputs: differential signal is amplified (Inputs #1 and #2), relative to a common reference (ground, input #3)




- Limb wires/electrodes connect to amplifier

ECG wires connect to amplifier circuit to human subject with stick-on skin electrodes

FUNCTIONS OF THE CIRCUIT (CON'T)

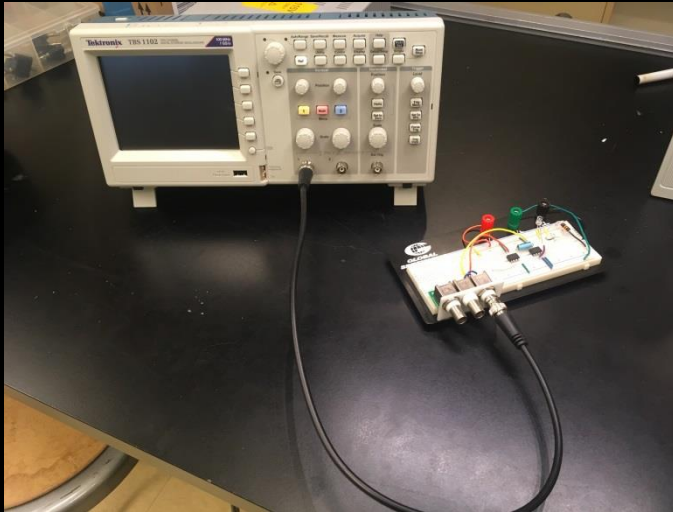- Output: Amplified ECG to “BNC” connector (part of the bread board)
 - Output can be viewed on an oscilloscope or computer acquisition system




BNC type “twist and lock” connector


Bread-boarded circuit using the BNC connector, via a co-axial cable, to the input of the oscilloscope

FUNCTIONS OF THE CIRCUIT (CON'T)

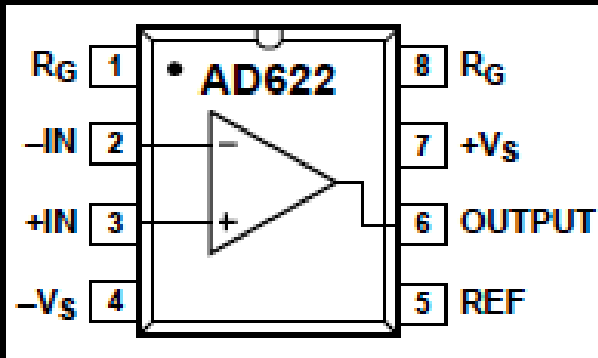- Main amplification
 - Voltage on the skin is in the millivolt range
 - Use the AD622 “differential” amplifier to boost signal to volt range
 - Amplifies the difference between the 2 inputs (-IN and +IN): will reject noise common to both inputs
 - Resistor between R_G pins sets amplification. $R = 100 \Omega$ is for gain of ~ 500 (Out = $500 \times$ In)



Pins on an 8-pin IC

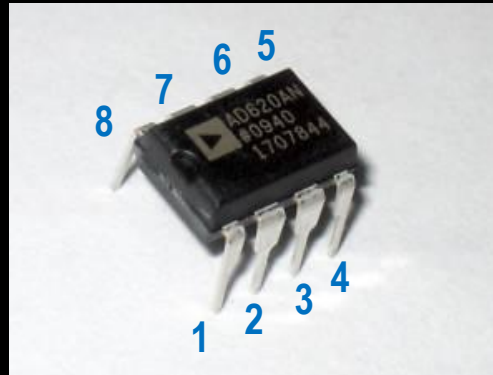

Pin functions


- 1 - Gain resistor
- 2 - Input #1
- 3 - Input #2
- 4 - Negative supply (-9V)
- 5 - no connections
- 6 - Amplified output
- 7 - Positive supply (+9V)
- 8 - Gain resistor

FUNCTIONS OF THE CIRCUIT (CON'T)

- Filters
 - Input filters: Low-pass (passes low frequencies, cuts out higher frequencies)
 - R-C combination at each input: $100\text{K } \Omega$ resistor with a 22 pico-farad capacitor
 - High pass filter: passes high frequency, filters out very low frequencies
 - R-C combination at AD622 output: $100\text{K } \Omega$ resistor with a 22 micro-farad capacitor
 - Active “band-pass” filter: filters around 60 Hz, which is frequency of household AC voltage/current. Major source of noise.
 - LM741 amplifier with $100\text{K } \Omega$, $150\text{K } \Omega$, $0.01 \mu\text{F}$.

LM 741: BASIC OPERATIONAL AMPLIFIER

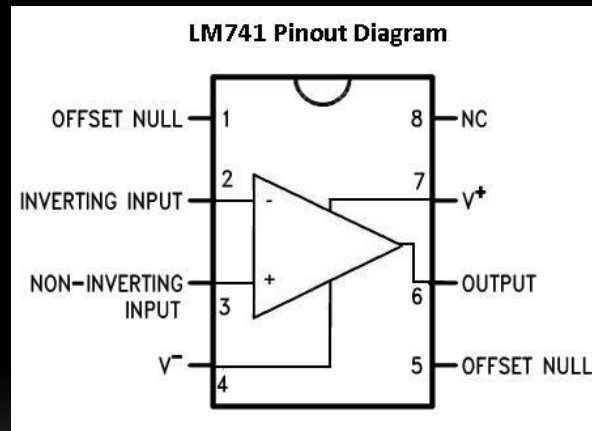- Basic amplifier used in many applications
 - Here, connected as the 60 Hz filter
 - Same pin order as the AD620
 - Same +/- 9V supplies on pins 4/7
 - Same input pins (2 and 3), and output pin (6)
 - Pins 1, 5, 8 not used in our configuration





RESISTORS

- Standard resistors use a 4-stripe “color code” for resistance value
 - First 2 bands are digits of the value, times the multiplier band. 4th band is tolerance

Resistor Color Table


1st Digit	2nd Digit	Multiplier	Tolerance
0	0	x 1 Ω	± 1%
1	1	x 10 Ω	± 2%
2	2	x 100 Ω	
3	3	x 1 KΩ	
4	4	x 10 KΩ	
5	5	x 100 KΩ	
6	6	x 1 MΩ	
7	7		± 5%
8	8	x 0.1 Ω	± 10%
9	9	x 0.01 Ω	

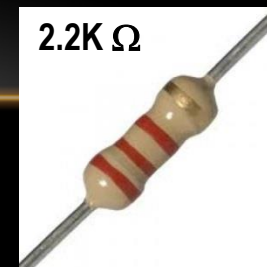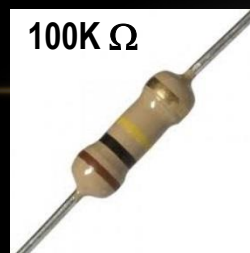- 100K Ω = Brown, Black, Yellow code. Tolerance is typically gold (5%) or silver (10%)
- 150K Ω = Brown, Green, Yellow; 100 Ω = Brown, Black, Brown
- “Precision” resistors, i.e. 1% tolerance, have value printed or 5-stripe code; precision = brown (1%)




CAPACITORS

- Many shapes and sizes. Some are polarized (electrolytic) with a labeled polarity.
- Capacitors use various codes for values. Mostly printed value is in “pico-Farads”
 - 1000 pico-farad (pF) = 1 nF = .001 μ F
 - Small caps use 3 digits: First 2 digits x multiplier 10^n , n = 3rd digit. i.e. “103” = $10 \times 10^3 = 10000$ pf (= .01 μ F)
 - 22 pF can also be written as “22” or “22K”, where K denotes the tolerance code (if only 2 digits, no multiplier).
 - Larger values of capacitance require the polarized capacitor type, with positive and negative ends. Most 22 μ F’s are polarized (note polarity in schematic).

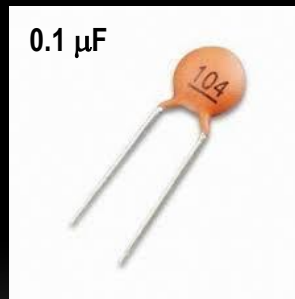

DIODES


- Diodes are a 1-way gate for current flow (current rectifier).
 - Small threshold for current flow ($<1\text{ V}$)
 - Therefore, if voltage is $>1\text{V}$, current will flow along arrow in schematic (anode to cathode)
 - Here, use for safety: any voltage $>1\text{ volt}$ on subject will flow through diode, not through the user!
 - Each pair protects against both positive and negative voltages.
 - Since ECG voltage is much less than 1V , it is not affected by diodes in normal operation

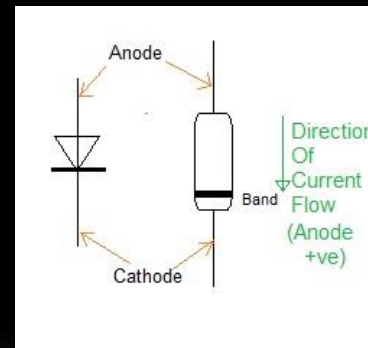

CREATE PARTS LIST WITH PICTURES IF NEEDED (SHOULD MATCH PARTS IN YOUR BAG!)

Sample (Partial) Parts List for ECG Amplifier

Resistors:

(1) 100 Ohm 

(4) 100K Ohm 1% 

Capacitors:

(1) 100 pF 

(1) 22uF 

Semiconductors

(4) 1N4004 Diodes 

(1) AD622 Chip

(1) LM741 Chip

WEEK 3 TOPICS FOR FINAL REPORT

- Schematic diagram of the electronic amplifier circuit.
 - Text description of the circuit functions, including 2 8-pin amplifiers.
 - Table of electronic components needed for the design, with images/pictures!
 - Include listing of additional parts such as bread board, batteries, etc.
-